

Name:

Date:

Science Assessment Year 4: Electricity

What is Electricity

1. Choose the correct word in each box to make this sentence right:





All things are made up of **microorganisms / atoms**. These help make electric **current/generators**.

1 mark

2. Name a way that we see electricity occurring naturally.

1 mark

3. Tick whether the bulb will be lit or not lit in each of these diagrams:

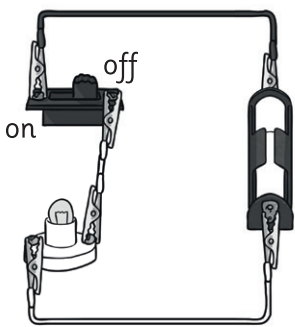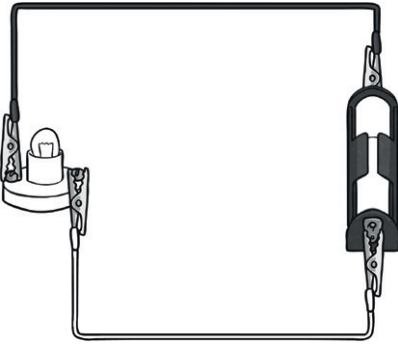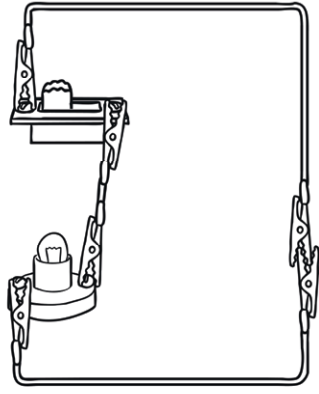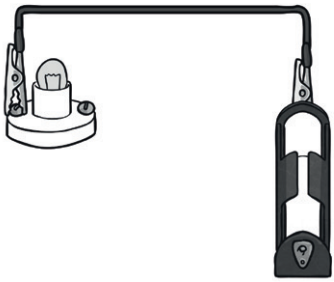 <p>Lit: <input type="checkbox"/> Not Lit: <input type="checkbox"/></p>	 <p>Lit: <input type="checkbox"/> Not Lit: <input type="checkbox"/></p>
 <p>Lit: <input type="checkbox"/> Not Lit: <input type="checkbox"/></p>	 <p>Lit: <input type="checkbox"/> Not Lit: <input type="checkbox"/></p>

4 marks

Total for this page

Everyday Electricity

4. Draw lines to match these items to **battery** or **mains** electricity:



Mains
Electricity

Battery
Electricity





3 marks

5. Name two ways of making electricity from a renewable source.

1 mark

Electrical Circuits

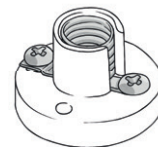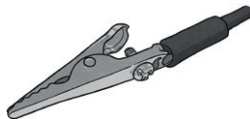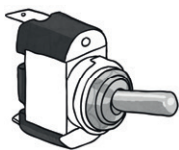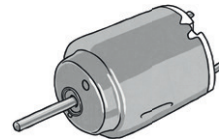
6. Name these pieces of equipment that you might use when you are making electrical circuits:



3 marks

Total for
this page

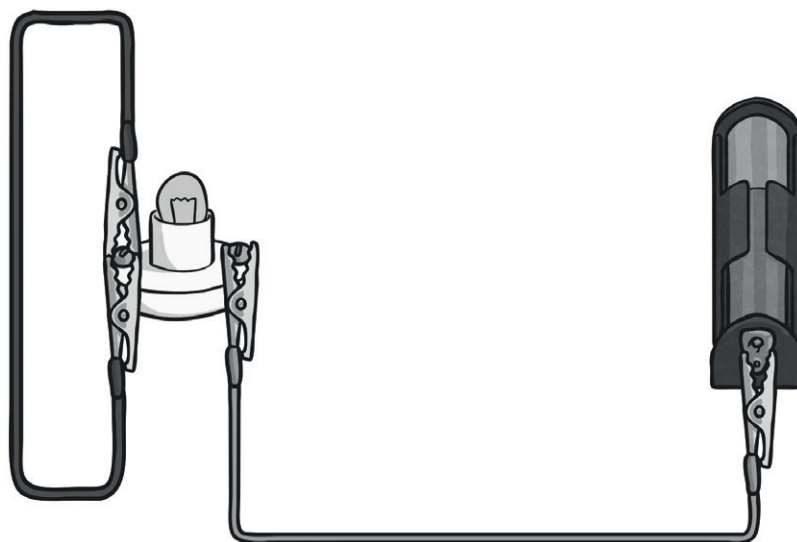7. Will the light bulb in this circuit light up? Explain why or why not:



Will it light up?

.....

Why?

.....

.....

.....

.....

1 mark


8. Why would you want to put a switch in a circuit?

.....


1 mark

Total for
this page

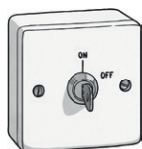9. Join up these pictures of switches to their name:




● slide switch

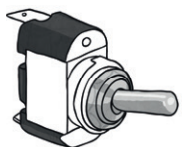

● push button switch




● pull switch

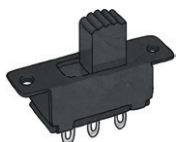


● dimmer switch



● rocker switch

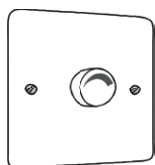

● selector switch

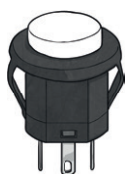

● key switch



● toggle switch

10. Why do most bathrooms have pull switches?

.....

.....


3 marks

2 marks

Total for this page

Electrical Investigation

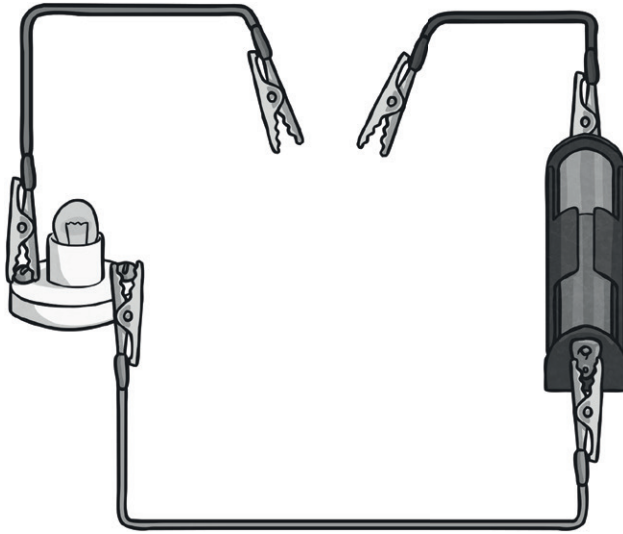A group of Year 4 children have made this circuit to test some different materials to see if they will conduct electricity or not:



11. What do the children mean when they say 'conduct electricity'?

.....

.....

1 mark

This is the table of results they got from their investigation:

	Does it light the bulb?
Wood	No
Copper wire	Yes
Paper	No
Plastic ruler	No
Paper clip	Yes

12. What is the independent variable that they are testing?

.....

1 mark

13. What should the title of the first column be?

.....

1 mark

Total for
this page

14. What do you notice about the materials that **do** conduct electricity?

1 mark

15. What is the name for a material that **does not** conduct electricity?

1 mark


Total for
this page

Answer Sheet: Science Assessment Year 4:

Electricity



question	answer	marks	notes
1. Choose the correct word in each box to make this sentence right.			
	All things are made up of atoms . These help make electric current .	1	
2. Name a way that we see electricity occurring naturally.			
	<ul style="list-style-type: none"> Static electricity (or an example of this) Lightning (Electric) eel 	1	
3. Tick whether the bulb will be lit or not lit in each of these diagrams:			
a	No (the switch is turned off)	1	
b	Yes	1	
c	No (There is no battery)	1	
d	No (Not a complete circuit)	1	
4. Draw lines to match these items to battery or mains electricity.			
		3	0 marks for 0-1 correct 1 mark for 2-3 correct 2 marks for 4-5 correct 3 marks for 6 correct
5. Name two ways of making electricity from a renewable source.			
	<ul style="list-style-type: none"> Wind turbines (not windmills) Hydroelectricity (or an example of this) Solar panels Tidal 	1	1 mark for any two correct.
6. Name these pieces of equipment that you might use when you are making electrical circuits.			
		3	0 marks for 0-1 correct 1 mark for 2-5 correct 2 marks for 6-8 correct 3 marks for 9 correct

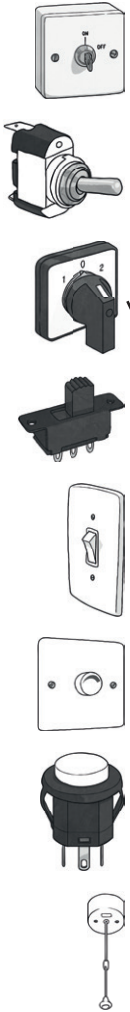question	answer	marks	notes
7. Will the light bulb in this circuit light up? Explain why.			
	<ul style="list-style-type: none"> No + it is an incomplete circuit No + there is a break/gap in the circuit No + the lamp/bulb is not joined to the battery/cell in a circuit 	1	<p>1 mark for no plus a correct explanation.</p> <p>In lessons make sure that 'incomplete' is the best vocabulary.</p>
8. Why would you want to put a switch in a circuit?			
	To turn it on/off	1	
9. Join up these pictures of switches to their name.			
	 <p>slide switch</p> <p>push button switch</p> <p>pull switch</p> <p>dimmer switch</p> <p>rocker switch</p> <p>selector switch</p> <p>key switch</p> <p>toggle switch</p>	3	<p>0 marks for 0-1 correct 1 mark for 2-5 correct 2 marks for 6-7 correct 3 marks for 8 correct</p>

question	answer	marks	notes
10. Why do most bathrooms have pull switches?			
	<ul style="list-style-type: none"> It is safer /for safety An understanding that water and electric mixed are dangerous. Bathrooms have water and water is dangerous when mixed with electricity so water is well away from the electric. Wet hands cannot touch electric switches so a pull switch keeps your hands away from the switch. 	2	1st mark 2nd mark Example 2 mark answers.
11. What do the children mean when they say 'conduct electricity'?			
	<ul style="list-style-type: none"> Completes the circuit by letting electricity pass through it Lets electricity easily pass through it Electricity can travel through it easily 	1	Make sure in lessons that children understand the real dangers of electricity and an 'insulator' does NOT give 100% protection from shock.
12. What is the independent variable that they are testing?			
	The material /what is going in the gap	1	
13. What should the title of the first column be?			
	<ul style="list-style-type: none"> Type of material Material 	1	
14. What do you notice about the materials that do conduct electricity?			
	<ul style="list-style-type: none"> They are metals 	1	Make sure that children know about non-metallic conductors such as water and graphite (graphite can be demonstrated shown using a pencil with 2 sharpened ends).
15. What is the name for a material that does not conduct electricity?			
	<ul style="list-style-type: none"> Insulator 	1	Make sure in lessons that children understand the real dangers of electricity and an 'insulator' does not give 100% protection from shock.
		total 25	